



# FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรแสบซิติวิทยุ AM ระบบไอซี พร้อมลำโพง  
AM RADIO IC RECEIVER EXPERIMENTAL BOARD  
CODE 713  
LEVEL 1

By utilizing a single IC AM to carry out both tuning and amplification of AM radio frequency, the construction time for FK713 is reduced to a minimum. This AM receiver is ideal for a class-room project when connected to the supplied speaker. If more powerful signal output is required ,many audio amplifiers from the Future Kit series can be conveniently applied.

#### ข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 6 โวลต์ดีชี
- กินกระแสสูงสุดประมาณ 70 มิลลิแอมป์
- ขนาดแผ่นวงจรพิมพ์ : 3.51 x 2.24 นิ้ว

#### การทำงานของวงจร

วงจรนี้แยกออกเป็น 2 ส่วนคือภาครับและภาคขยาย IC ทำหน้าที่ เป็นภาครับ โดยมี VC (วาริเอเบิล) และ COIL เป็น ตัวปรับ habitats สถานีที่รับได้จะถูกนำเข้าไปขยาย โดยใช้ไอซี และส่งออกทางขา OUT ผ่าน R และ C มาเข้า VR1 นี้จะทำหน้าที่เร่งดัง หรือเสียงที่ขา กองของวงจรลุ่มจะตอบเข้ามา 3 ของไอซี ซึ่งเป็นอินพุทของไอซีภาค ขยายเสียง เพื่อทำการขยาย ออกลำโพงต่อไป

#### การประกอบวงจร

รูปการลงอุปกรณ์แสดงไว้ในรูปที่ 1 ในการประกอบวงจร ควรจะ เริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วยตัวด้านบนและໄล ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีชั้วๆ เช่น ไดโอด คากาชิสเตอร์ แบบอิเล็กทร็อกและทรานซิสเตอร์ เป็นต้น ควรใช้ความระมัดระวังในการประกอบวงจร ก่อนการใส่อุปกรณ์เหล่านี้จะต้องให้ชั้วที่ แห้งๆ ของรินพกับตัวอุปกรณ์ให้ตรงกัน เพราะถ้าหากใส่กลับขึ้นแล้ว อาจจะทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการดูชั้วและการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 2 และ ในการบัดกรีให้หัวแร้งขนาดไม่เกิน 40 วัตต์ และใช้ตะเก็บบัดกรีที่มีอัตราส่วนของดีบุกและตะกั่วอยู่ระหว่าง 60:40 รวมทั้งจะต้องมีน้ำยาประสานอยู่ภายในตะกั่วด้วย หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ทำการตรวจสอบความถูกต้องอีกรอบหนึ่ง แต่ถ้าเกิดใส่อุปกรณ์ผิดตำแหน่ง ควรใช้ที่ดูดตะกั่วหรือดูดซับตะกั่ว เพื่อป้องกันความเสียหายที่อาจเกิดกับสายวงจรพิมพ์ได้

#### การทดสอบ

จ่ายไฟเข้าวงจรซึ่งวงจนี้ใช้ไฟดังเดี่ย 6 โวลต์ ให้หมุนหาสถานีที่ ความถี่สูงที่สุดโดยหาวิทยุมาเปิดเทียบดู สถานีสูงสุดไม่มีอยู่ในตำแหน่งสูงสุด ให้หมุนวาริเอเบิลไปทางที่สถานีสูงสุด ตอนนี้จะไม่มี สถานีวิทยุ ให้ห้าวิเคราะห์ปรับทริมเมอร์ตรงจุด G เล็กน้อย สถานีสูงสุด ที่รับได้ก่อนหน้านี้จะมาอยู่ในตำแหน่งวาริเอลามบูสต์

**หมายเหตุ:** ในการทดสอบวงจรและการนำไปใช้งาน ควรกระทำในพื้นที่โล่งแจ้ง เพื่อการรับสัญญาณที่ดี

# วงจรแสบซิติวิทยุ AM ระบบไอซี พร้อมลำโพง

AM RADIO IC RECEIVER EXPERIMENTAL BOARD

CODE 713

By utilizing a single IC AM to carry out both tuning and amplification of AM radio frequency, the construction time for FK713 is reduced to a minimum. This AM receiver is ideal for a class-room project when connected to the supplied speaker. If more powerful signal output is required ,many audio amplifiers from the Future Kit series can be conveniently applied.

#### Technical data

- Power supply : 6 VDC.
- Electric current consumption : 70 mA. (max.).
- IC board dimension : 3.51 in x 2.24 in.

#### How does it work

This circuit consist of two sections; receiver and amplifier. IC will function as a self-contain receiver with the help of VC (variable capacitor) and coil. The received signal after pre-amplified by IC will be transmitted via the "OUT" pin to VR 1 (with R and C along the way). The output of VR1 is then feed directly to pin 3 of IC for further amplification work . This signal (can also be adjusted by VR1) can be heard when connected to the supplied speaker.

#### Circuit Assembly





The assembly of components is shown in Fig. 1. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 2. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

#### Testing

Energize the circuit with 6VDC. Turn the turning knob (VC) to the extreme clockwise position and verify whether there is a signal of the highest AM radio(station) frequency come out by comparing it to the house hold radio nearby. If not ,use a screw to adjust the trimmer (at "G" spot) until it does.

**Note:** For testing and using the circuit, should be done in the open air. In order to receive the radio signal as well.

Figure 1. The AM Radio IC Receiver Experimental Board Circuit

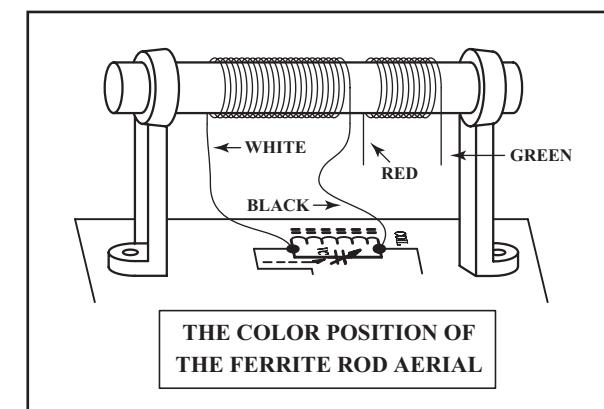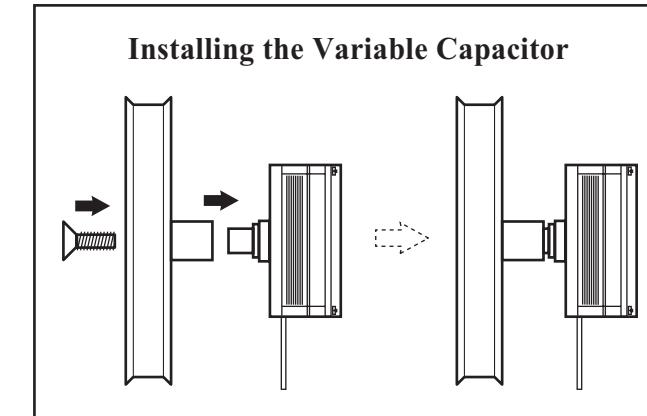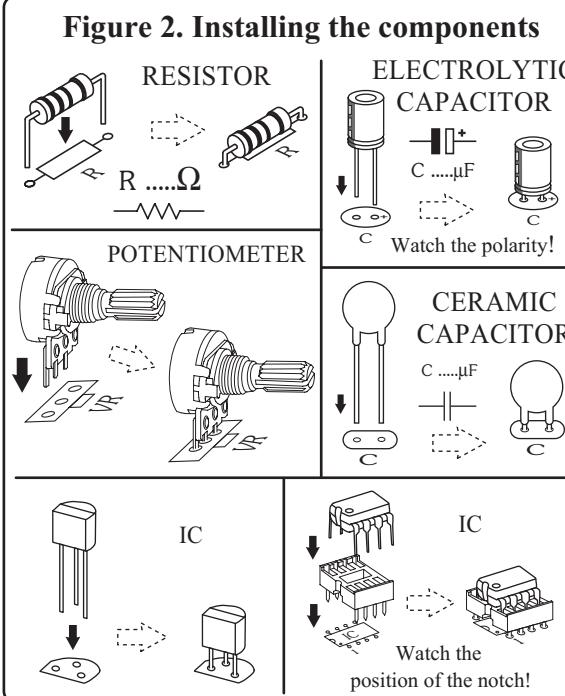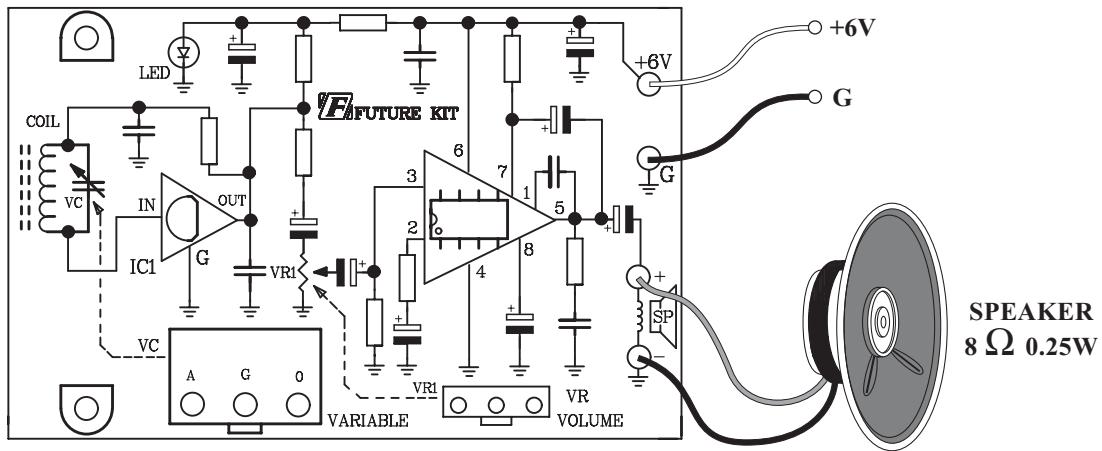

**NOTE:**  
FUTURE BOX FB04 is suitable for this kit.